


# Sequential logic

- Sequential logic has memory: past values of a signal influence the present values
- We add a way for the past to influence the present: a Delay gate

$S = a_0 | a_1 | a_2 | \dots | a_i | \dots$


$T = b_0 | b_1 | b_2 | \dots | b_i | \dots$

$b_i = a_{i-1} \Rightarrow T = 0 | S$

 


**fun** {DelayG S} 0 | S **end**

# Latch specification

 

- A latch is a simple circuit with memory; it has two stable states and can memorize its input
- Output  $d_o$  follows input  $d_i$  and freezes when  $c$  is 1

# Latch implementation

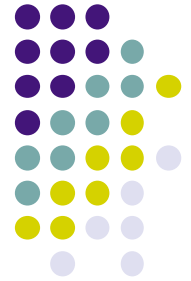

- Latch creation as a three-argument component:

```
proc {Latch C Di Do}
```

```
  A B E F
```

```
in
```

```
  F={DelayG Do}
```

```
  A={AndG C F}
```

```
  E={NotG C}
```

```
  B={AndG E Di}
```

```
  Do={OrG A B}
```

```
end
```